

Nicolas Rampelotto and Jason Pritchett:

Modifications Made:

- 1) Removed extra semicolon from line 6
- 2) Removed is\_prime from last line and replaced with equations.
- 3) Added semicolon to ending the entity
- 4) Added parenthesis surrounding the NOT a AND b AND d

Error Messages From Adding 0 and 1 Minterms to Logic Description:

Warning: Circuit failed for abcd=0000

Warning: Circuit failed for abcd=0001

SS For Working Prime Number Circuit:

